

In this homework we have five project options. You only need to pick one of them and finish it completely using full-custom approach. Your report must at least include circuit, layout, pre-layout and post-layout simulation results, LVS result, and DRC result. Also you may add I/O pads to your circuit core and run off-line DRC.

**Project 1:** Design and implement an  $4 \times 4$  Booth's array multiplier (Slide 12-59) studied in the class.

**Project 2:** Design and implement an 8-bit synchronous binary counter.



**Project 3:** Design and implement an 8-bit carry-lookahead adder.

**Project 4:** Design and implement an 8-bit carry-skip adder.


**Project 5:** Design and implement the non-restoring array divider (Slides 12-63 and 12-64) studied in the class.

此次作業選擇 project 2:實作一個 8 bit 的二元計數器。

初步設計:透過 8 個 JK 正反器搭配 AND 來實現計數器。

  



透過 D 型正反器來實現 JK 正反器。

 


D 型正反器。

實作:


JK 正反器-schematic。

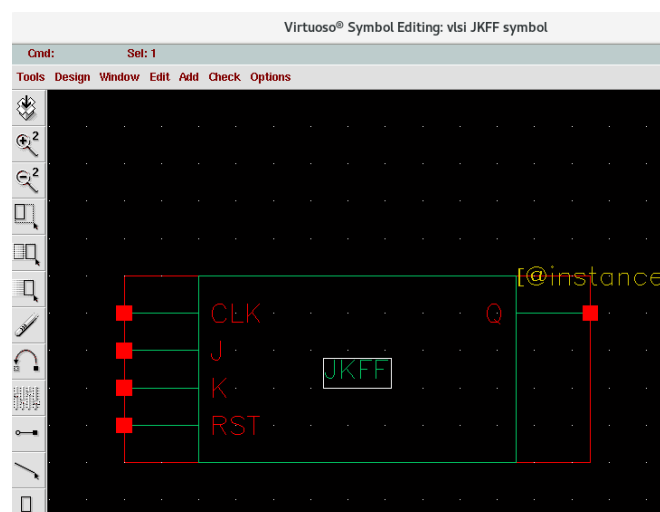 

將 JK 正反器設定成 symbol  
方便後續設計計數器。

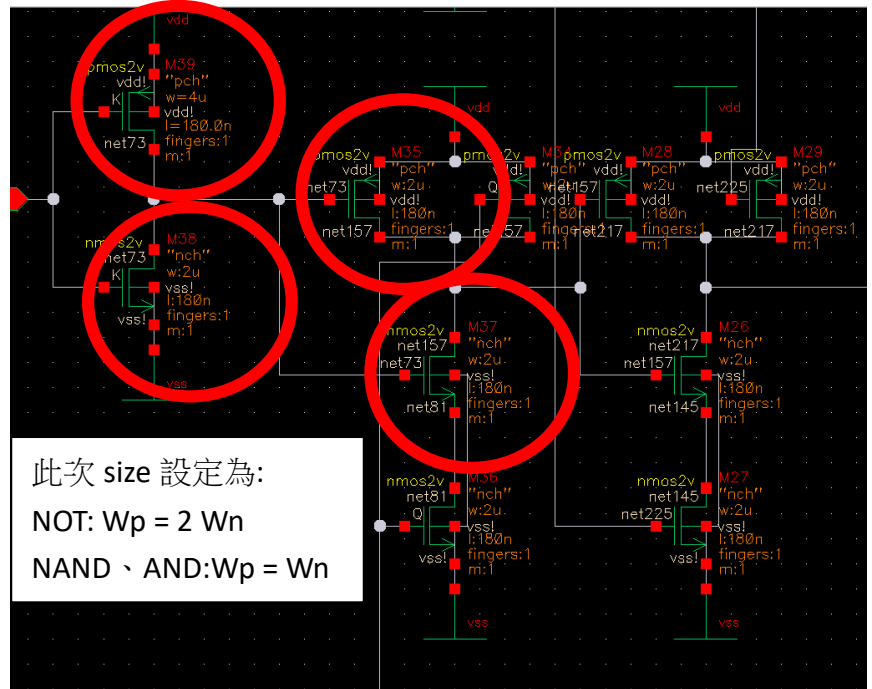

JK 正反器功能測試

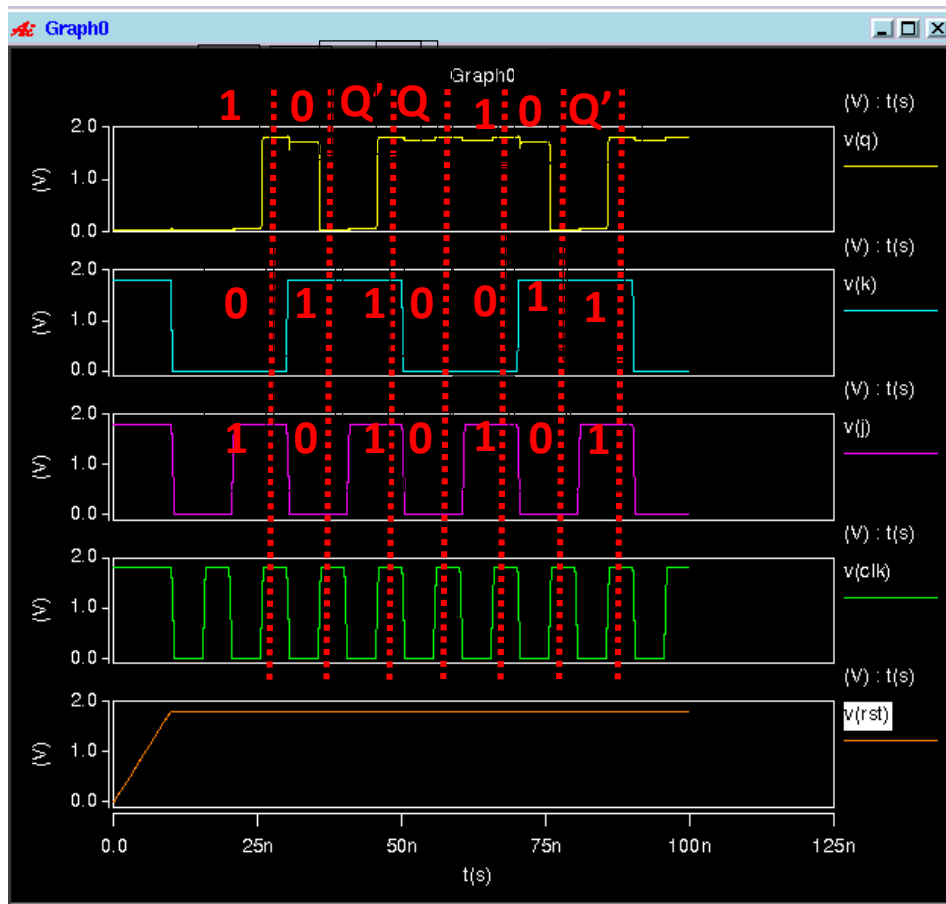

Truth Table

CLK	J	K	$Q_{n+1}$
↑	0	0	$Q_n$
↑	0	1	0
↑	1	0	1
↑	1	1	$Q_n'$

JK layout


SP 檔(無測 delay)

```
*JKFF.sp
~cic018/spfile

MM7 net183 CLK vdd! vdd! pmos l=180n w=2u m=1
MM8 net177 net217 vdd! vdd! pmos l=180n w=2u m=1
MM9 net177 net181 vdd! vdd! pmos l=180n w=2u m=1
MM12 net181 net183 vdd! vdd! pmos l=180n w=2u m=1
MM13 net181 net177 vdd! vdd! pmos l=180n w=2u m=1
MM14 net181 CLK vdd! vdd! pmos l=180n w=2u m=1
MM20 0 net183 vdd! vdd! pmos l=180n w=2u m=1
MM21 0 net227 vdd! vdd! pmos l=180n w=2u m=1
MM22 net227 0 vdd! vdd! pmos l=180n w=2u m=1
MM23 net227 net181 vdd! vdd! pmos l=180n w=2u m=1
MM40 net183 RST vdd! vdd! pmos l=180n w=2u m=1
MM42 net177 RST vdd! vdd! pmos l=180n w=2u m=1
MM0 net167 net183 vdd! vdd! pmos l=180n w=2u m=1
MM1 net167 net177 vdd! vdd! pmos l=180n w=2u m=1
MM20 net217 net157 vdd! vdd! pmos l=180n w=2u m=1
MM29 net217 net225 vdd! vdd! pmos l=180n w=2u m=1
MM32 net225 net227 vdd! vdd! pmos l=180n w=2u m=1
MM33 net225 J vdd! vdd! pmos l=180n w=2u m=1
.ENDS

.lib "PTM180.L" cmos
xJKFF CLK J K Q RST JKFF
vdd vdd! 0 1.8
vss vss! 0 0
VCLK CLK 0 pulse( 1.8 0 10n 0.5n 0.5n 4.9n 10n )
VJ J 0 pulse( 1.8 0 10n 0.5n 0.5n 9.9n 20n )
VK K 0 pulse( 1.8 0 10n 0.1n 0.1n 19.9n 40n )
VRST RST 0 PWL(0n 0v 10n 1.8v)
.trans lps 100ns

 .probe tran V(CLK) V(J) V(K) V(RST) V(Q)
.option post=2
.end
```



DRC:全為 density 問題(忽略)

Calibre - RVE v2021.1\_33.19: JKFF.drc.results

Filter: Show Not Waived JKFF, 7 Results (in 7 of 366 Checks)

- Check / Cell
- Check NO.IND.P0.R.3
- Check NO.IND.M1.R.1
- Check NO.IND.M2.R.1
- Check NO.IND.M3.R.1
- Check NO.IND.M4.R.1
- Check NO.IND.M5.R.1
- Check UTM20K.R.1

LVS Report File - JKFF.lvs.report

LVS :->

REPORT FILE NAME: JKFF.lvs.report  
LAYOUT NAME: /home/vlsi24f/m11302155/cic018/JKFF.sp ('JKFF')  
SOURCE NAME: /home/vlsi24f/m11302155/cic018/spfile/JKFF.sp.bak ('JKFF.sp.bak')  
RULE FILE: /home/vlsi24f/m11302155/cic018/spfile/lvs\_rules.lvs\_  
CREATION TIME: Fri Dec 6 21:24:29 2024  
CURRENT DIRECTORY: /home/vlsi24f/m11302155/cic018  
USER NAME: m11302155  
CALIBRE VERSION: v2021.1\_33.19 Mon Mar 1 16:10:01 PST 2021


OVERALL COMPARISON RESULTS

CORRECT

JKFF.lvs.report.ext  
 JKFF.pex.sp  
 JKFF.pex.sp.JKFF.pxi  
 JKFF.pex.sp.pex

PEX :檔案如圖

PEX :測試波形

 

```

*JKFF.pex.sp
~tsc018/pex




+ NRS=0.135
mX39/M0 N 8 X39/M0 d N_CLK_X39/M0 g N_VDD! X39/M0 s N_VDD! X37/M1 b pmos
+ L=1.8e-07 W=2e-06 AD=9.6e-13 AS=5.4e-13 PD=4.96e-06 PS=2.54e-06 NRD=0.24
+ NRS=0.135
mX39/M1 N 8 X39/M1 d N_13 X39/M1 g N_VDD! X39/M1 s N_VDD! X37/M1 b pmos L=1.8e-07
+ W=2e-06 AD=5.4e-13 AS=9.6e-13 PD=2.54e-06 PS=4.96e-06 NRD=0.135 NRS=0.24
mX39/M2 N_VDD! X39/M2 d N_14 X39/M2 g N_8 X39/M2 s N_VDD! X37/M1 b pmos L=1.8e-07
+ W=2e-06 AD=5.4e-13 AS=5.4e-13 PD=2.54e-06 PS=2.54e-06 NRD=0.135 NRS=0.135
mX40/M0 N 6 X40/M0 d N_RST_X40/M0 g N_VDD! X40/M0 s N_VDD! X37/M1 b pmos
+ L=1.8e-07 W=2e-06 AD=9.6e-13 AS=5.4e-13 PD=4.96e-06 PS=2.54e-06 NRD=0.24
+ NRS=0.135
mX40/M1 N 6 X40/M1 d N_8 X40/M1 g N_VDD! X40/M1 s N_VDD! X37/M1 b pmos L=1.8e-07
+ W=2e-06 AD=5.4e-13 AS=9.6e-13 PD=2.54e-06 PS=4.96e-06 NRD=0.135 NRS=0.24
mX40/M2 N_VDD! X40/M2 d N_0 X40/M2 g N_6 X40/M2 s N_VDD! X37/M1 b pmos L=1.8e-07
+ W=2e-06 AD=5.4e-13 AS=5.4e-13 PD=2.54e-06 PS=2.54e-06 NRD=0.135 NRS=0.135
*
.include "JKFF.pex.sp.JKFF.pxi"
*
.ends
*
*
.Lib "PTM180.l" cmos
xJKFF K Q J RST CLK VSS! VDD! JKFF
vdd vdd! 0 1.8
vss vss! 0 0
VCLK CLK 0 pulse( 1.8 0 10n 0.5n 0.5n 4.9n 10n )
VJ J 0 pulse( 1.8 0 10n 0.5n 0.5n 9.9n 20n )
VK K 0 pulse( 1.8 0 10n 0.1n 0.1n 19.9n 40n )
VRST RST 0 PWL(0n 0v 10n 1.8v)
.trans lps 100ns


.probe tran V(CLK) V(J) V(K) V(RST) V(Q)
.option post=2
.end
  
```

SP 檔(無測  
delay)

AND 如同右圖(之前作業有透過 NAND 練習)，一樣透過創立 symbol 的方式，方便後續呼叫(AND 並沒有額外測試 DRC、LVS 等)。

波形圖如下

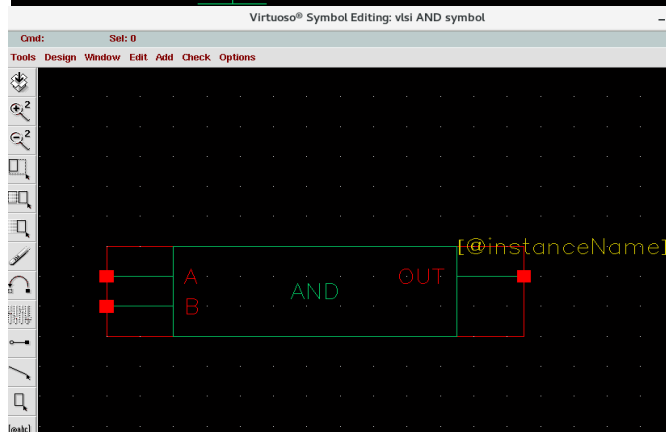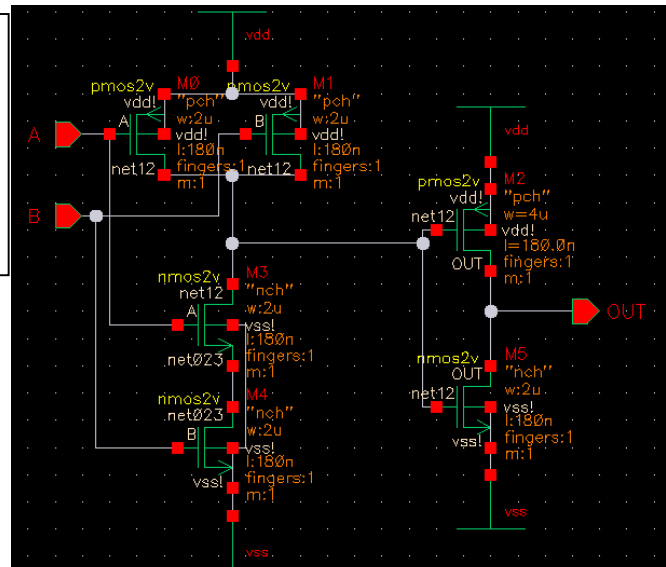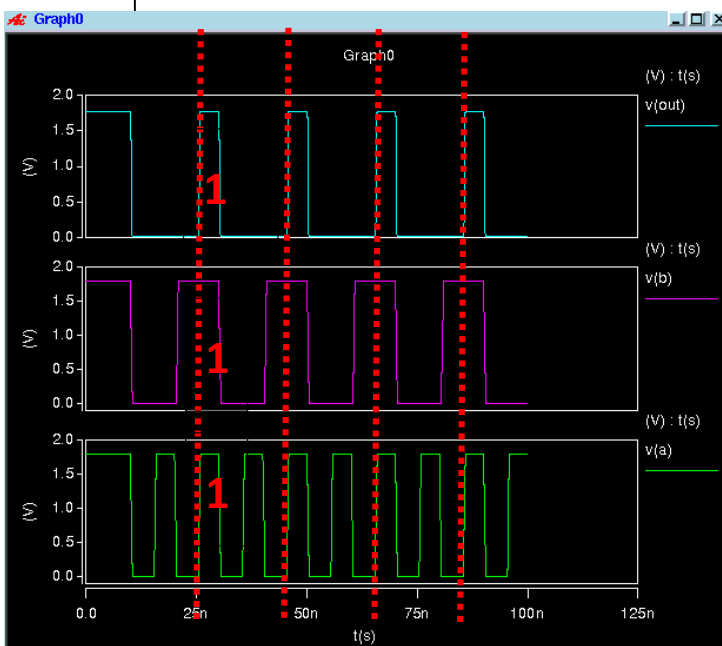

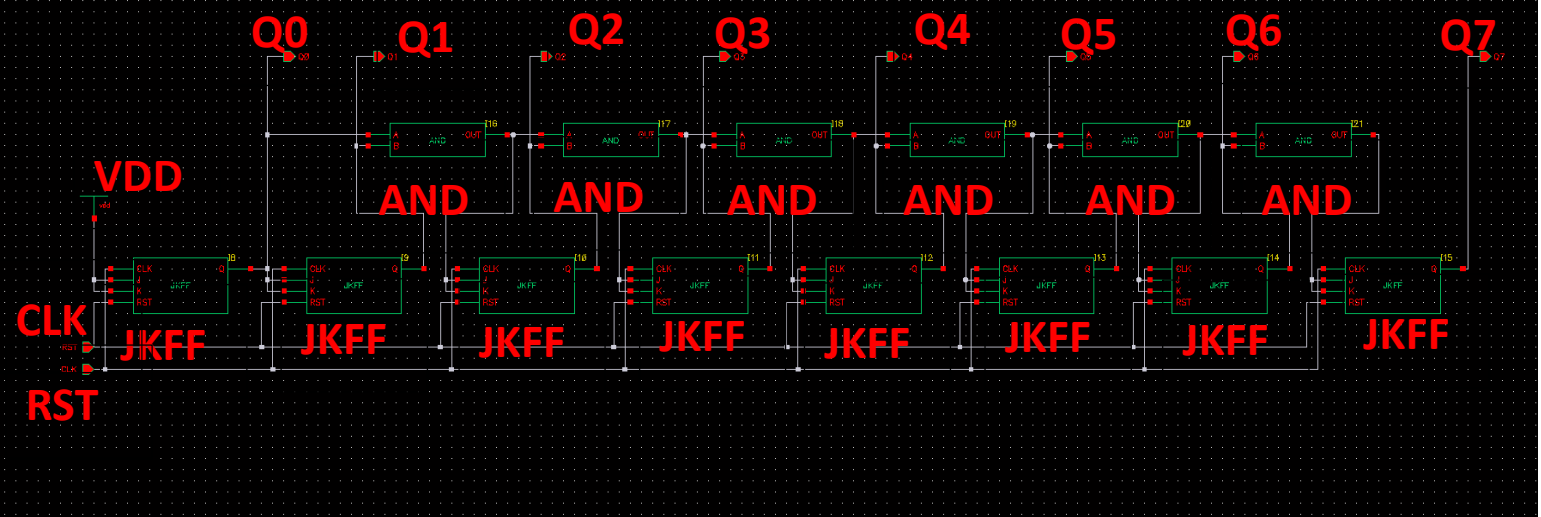

Open \*bit8\_syn\_binary\_counter.sp  
~cic018/spfile

```

*****
* Library Name: vlsi
* Cell Name:   bit8_syn_binary_counter
* View Name:   schematic
*****

.SUBCKT bit8_syn_binary_counter CLK Q0 Q1 Q2 Q3 Q4 Q5 Q6 Q7 RST
*.PININFO CLK:I RST:I Q0:0 Q1:0 Q2:0 Q3:0 Q4:0 Q5:0 Q6:0 Q7:0
XI16 Q0 Q1 net131 / AND
XI18 net125 Q3 net119 / AND
XI17 net131 Q2 net125 / AND
XI20 net107 Q5 net137 / AND
XI19 net119 Q4 net107 / AND
XI21 net137 Q6 net143 / AND
XI8 CLK vdd! vdd! Q0 RST / JKFF
XI13 CLK net107 net107 Q5 RST / JKFF
XI9 CLK Q0 Q0 Q1 RST / JKFF
XI12 CLK net119 net119 Q4 RST / JKFF
XI11 CLK net125 net125 Q3 RST / JKFF
XI10 CLK net131 net131 Q2 RST / JKFF
XI14 CLK net137 net137 Q6 RST / JKFF
XI15 CLK net143 net143 Q7 RST / JKFF
.ENDS


.lib "PTM180.l" cmos
xbit8_syn_binary_counter CLK Q0 Q1 Q2 Q3 Q4 Q5 Q6 Q7 RST bit8_syn_binary_counter
vdd vdd! 0 1.8
vss vss! 0 0
vCLK CLK 0 pulse (0 1.8 0 0.1n 0.1n 0.3n 1n)
VRST RST 0 PWL(0n 0v 5n 1.8v)
.trans 1ps 200ns

.probe tran V(CLK) V(RST) V(Q0) V(Q1) V(Q2) V(Q3) V(Q4) V(Q5) V(Q6) V(Q7)
.option post=2
.end


```

SP 檔(無測  
delay)

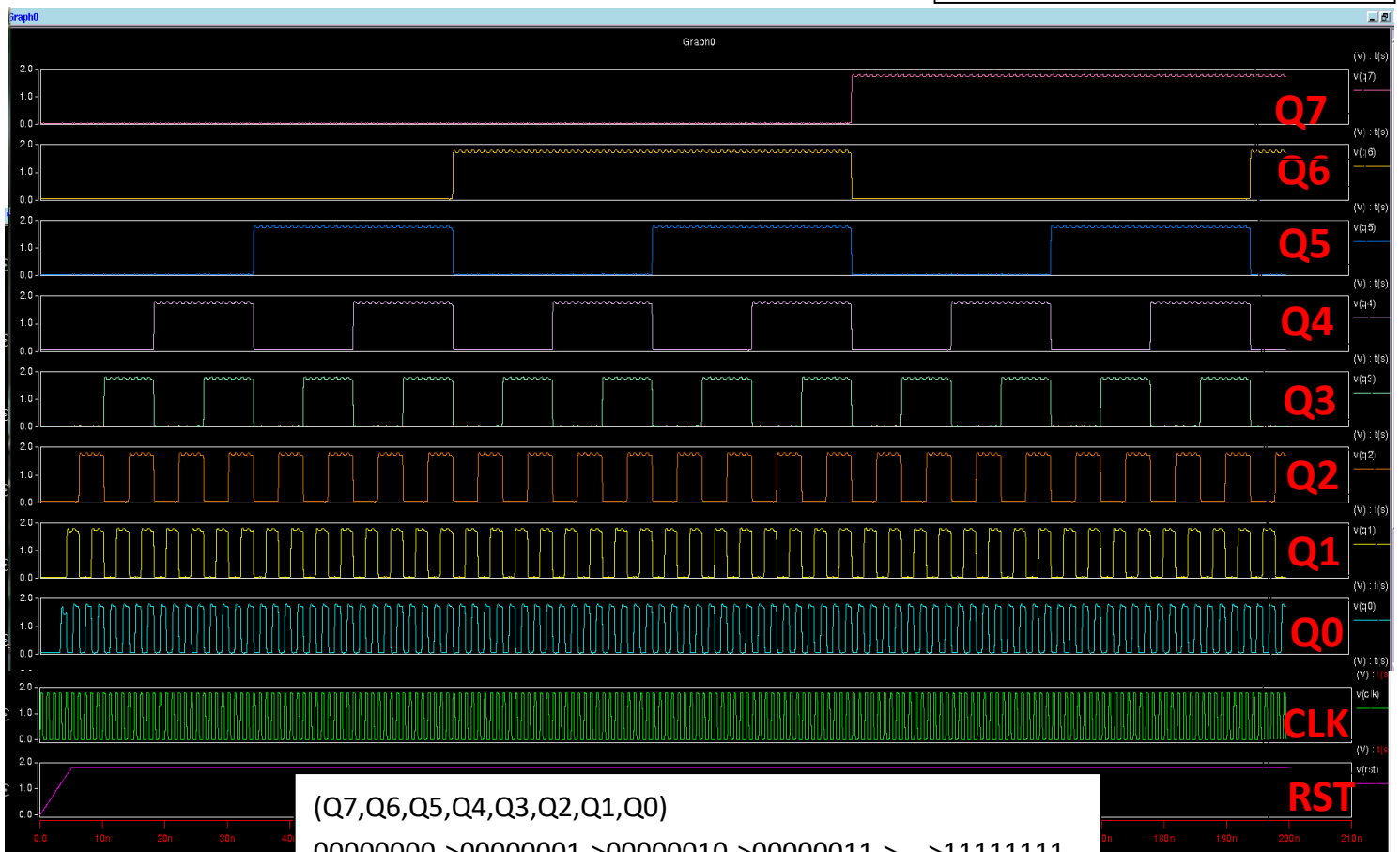可以看到每個  $Q_{n+1}$  的頻率都是  
 $Q_n$  的 1/2 倍。





 

整體  
layout

Calibre - RVE v2021.1\_33.19 : bit8\_syn\_binary\_counter.drc.results

File View Highlight Tools Window Setup Help

Filter: Show Unresolved bit8\_syn\_binary\_counter, 7 Results (in 7 of 366 Checks)

- Check / Cell
- Check NO.IND.PO.R.3
- Check NO.IND.M1.R.1
- Check NO.IND.M2.R.1
- Check NO.IND.M3.R.1
- Check NO.IND.M4.R.1
- Check NO.IND.M5.R.1
- Check UTM20K.R.1

DRC:全為 density  
問題(忽略)

NO.IND.PO.R.3 { @ Min. density of POLY area >= 14% (exclude application for inductor)  
ALL\_POLY\_NIND = POLY1 OR DPO  
POLY1\_NIND = ALL\_POLY\_NIND NOT INDDMY  
CHIP\_NIND = CHIP NOT INDDMY

LVS Report File - bit8\_syn\_binary\_counter.lvs.report

File Edit Options Windows

LVS :->

REPORT FILE NAME: bit8\_syn\_binary\_counter.lvs.report  
LAYOUT NAME: /home/vlsi24f/ml1302155/cic018/bit8\_syn\_binary\_counte  
SOURCE NAME: /home/vlsi24f/ml1302155/cic018/vpfile/bit8\_syn\_binary  
RULE FILE: /home/vlsi24f/ml1302155/cic018/\_libre.lvs\_  
CREATION TIME: Fri Dec 6 21:44:19 2024  
CURRENT DIRECTORY: /home/vlsi24f/ml1302155/cic018  
USER NAME: ml1302155  
CALIBRE VERSION: v2021.1\_33.19 Mon Mar 1 16:10:01 PST 2021

OVERALL COMPARISON RESULTS


#####  
#  
# CORRECT #  
#  
#####

CELL SUMMARY

Edit Row 25 Col 25

bit8\_syn\_binary\_counter.calibre.db  
bit8\_syn\_binary\_counter.lvs.report.ext  
bit8\_syn\_binary\_counter.pex.ic0  
bit8\_syn\_binary\_counter.pex.lis  
bit8\_syn\_binary\_counter.pex.mt0  
bit8\_syn\_binary\_counter.pex.pa0  
bit8\_syn\_binary\_counter.pex.sp  
bit8\_syn\_binary\_counter.pex.sp.BIT8\_SYN\_BINARY\_COUNTER.pxi  
bit8\_syn\_binary\_counter.pex.sp.pex  
bit8\_syn\_binary\_counter.pex.st0  
bit8\_syn\_binary\_counter.pex.tr0

PEX :檔案如圖

Open 

\*bit8\_syn\_binary\_counter.pex.sp  
~fci018/pex

mX125/X17/M0 N\_78\_X125/X17/M0\_d N\_CLK\_X125/X17/M0\_g N\_VDD!\_X125/X17/M0\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=9.6e-13 AS=5.4e-13 PD=4.96e-06  
+ PS=2.54e-06 NRD=0.24 NRS=0.135  
mX125/X17/M1 N\_78\_X125/X17/M1\_d N\_89\_X125/X17/M1\_g N\_VDD!\_X125/X17/M1\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=5.4e-13 AS=9.6e-13 PD=2.54e-06  
+ PS=4.96e-06 NRD=0.135 NRS=0.24  
mX125/X17/M2 N\_VDD!\_X125/X17/M2\_d N\_92\_X125/X17/M2\_g N\_78\_X125/X17/M2\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=5.4e-13 AS=5.4e-13 PD=2.54e-06  
+ PS=2.54e-06 NRD=0.135 NRS=0.135  
mX125/X18/M0 N\_74\_X125/X18/M0\_d N\_RST\_X125/X18/M0\_g N\_VDD!\_X125/X18/M0\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=9.6e-13 AS=5.4e-13 PD=4.96e-06  
+ PS=2.54e-06 NRD=0.24 NRS=0.135  
mX125/X18/M1 N\_74\_X125/X18/M1\_d N\_78\_X125/X18/M1\_g N\_VDD!\_X125/X18/M1\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=5.4e-13 AS=9.6e-13 PD=2.54e-06  
+ PS=4.96e-06 NRD=0.135 NRS=0.24  
mX125/X18/M2 N\_VDD!\_X125/X18/M2\_d N\_Q3\_X125/X18/M2\_g N\_74\_X125/X18/M2\_s  
+ N\_VDD!\_X71/M0\_b pmos L=1.8e-07 W=2e-06 AD=5.4e-13 AS=5.4e-13 PD=2.54e-06  
+ PS=2.54e-06 NRD=0.135 NRS=0.135  
\*  
.include "bit8\_syn\_binary\_counter.pex.sp.BIT8\_SYN\_BINARY\_COUNTER.pxi"  
\*  
.ends  
\*  
\*  
  
.lib "PTM180.l" cmos  
xbit8\_syn\_binary\_counter VDD! Q0 Q6 Q4 Q2 RST CLK Q1 Q7 Q5 Q3 VSS! bit8\_syn\_binary\_counter  
vdd vdd! 0 1.8  
vss vss! 0 0  
vCLK CLK 0 pulse (0 1.8 0 0.1n 0.1n 0.3n 1n)  
VRST RST 0 PWL(0n 0v 5n 1.8v)  
.trans lps 200ns  
  
.probe tran V(CLK) V(RST) V(Q0) V(Q1) V(Q2) V(Q3) V(Q4) V(Q5) V(Q6) V(Q7)  
.option post=2  
.end

SP 檔(無測 delay)

PEX 後的波形與前模擬一樣

